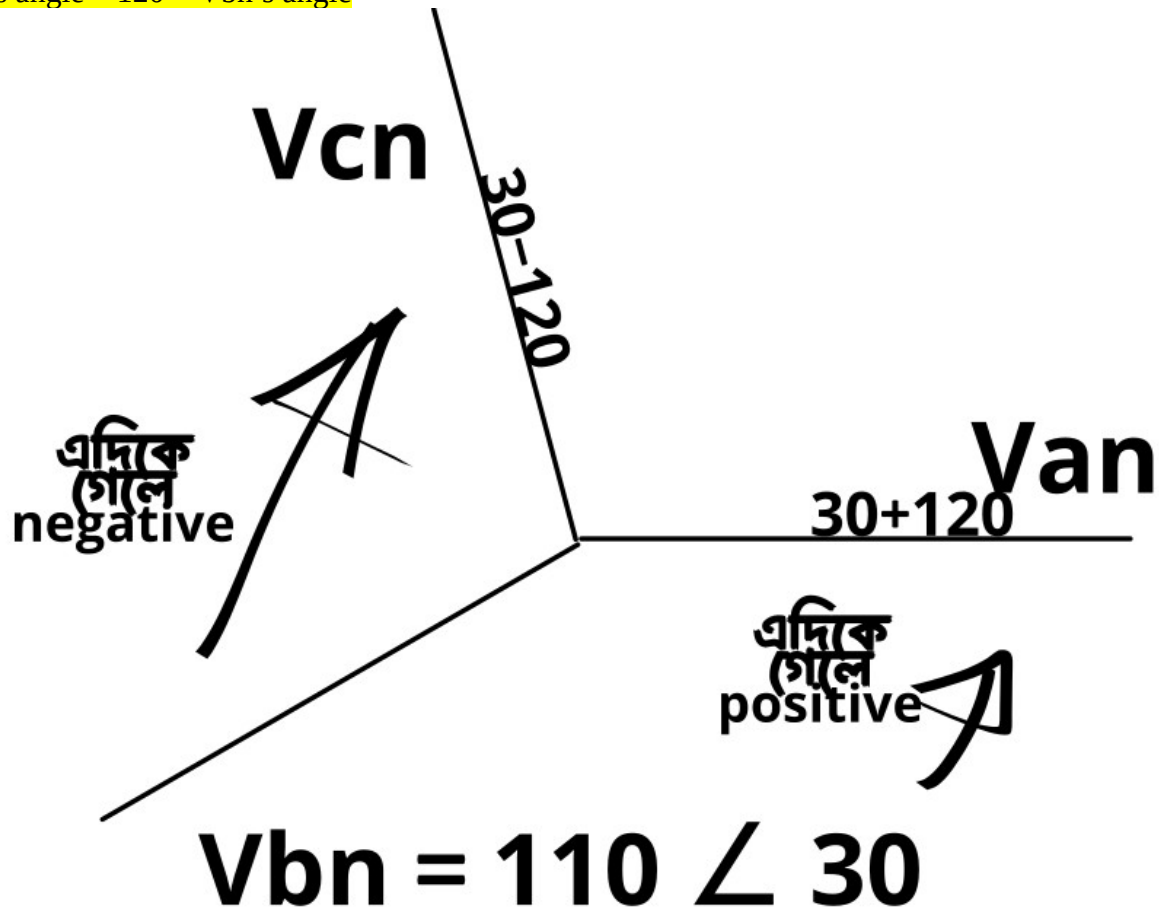


EEE | Practice problems (3-phase)

12.1 Given that $V_{bn} = 110 \angle 30$, find V_{an} and V_{cn} , assuming a positive (abc) sequence.

Van's angle $- 120 = V_{bn}$'s angle



12.2 A Y-connected balanced three-phase generator with an impedance of $0.4 + j0.3$ ohm per phase is connected to a Y-connected balanced load with an impedance of $24 + j19$ ohm per phase. The line joining the generator and the load has an impedance of $0.6 + j0.7$ ohm per phase. Assuming a positive sequence for the source voltages and that $V_{an} = 120 \angle 30$ V, find: (a) the line voltages, (b) the line currents.

Line voltages = $\sqrt{3}$ x phase voltage + phase shift by $\angle 30$

$$(a) \text{ for } V_{ab} (\text{line vol}) = \sqrt{3} \times 120 \angle (30+30) = 207.85 \angle 60$$

$$\text{অনুরূপভাবে, } V_{bc} = 207.85 \angle (60-120)$$

$$V_{ca} = 207.85 \angle (60-(2 \times 120)) \text{ অথবা, } 207.85 \angle (60+120)$$

^ (বই এ এভাবে করা আছে যদিও)

Line current = Phase current =

$$I_{ab} = \frac{V_{ab}}{0.4 + j0.3 + 24 + j19 + 0.6 + j0.7} = \frac{120 \angle 30}{0.4 + j0.3 + 24 + j19 + 0.6 + j0.7} = 3.7 \angle -8.66 \text{ A}$$

$$\text{Likewise, } I_{bc} = 3.7 \angle -128.66, I_{ca} = 3.7 \angle 111.34$$

12.3 One line voltage of a balanced Y-connected source is $V_{AB} = 240 \angle 20^\circ \text{ V}$. If the source is connected to a delta-connected load of $20 \angle 40^\circ \text{ ohm}$, find the phase and line currents. Assume the abc sequence.

Phase current,

$$I_{ab} = \frac{240 \angle -20}{20 \angle 40} = 12 \angle -60$$

$$I_{BC} = 12 \angle (-60 - 120) = 12 \angle -180$$

$$I_{CA} = 12 \angle (-60 + 120) = 12 \angle 60$$

Line currents,

$$I_a = \sqrt{3} \times I_{ab} \times \angle (-30) = \sqrt{3} \times 12 \angle (-60 - 30) = 20.78 \angle -90 \text{ A}$$

$$I_b = 20.78 \angle -210$$

$$I_c = 20.78 \angle 30$$

12.4 A positive-sequence, balanced delta-connected source supplies a balanced delta-connected load. If the impedance per phase of the load is $18 + j12 \text{ ohm}$ and $I_a = 19.202 \angle 35^\circ \text{ A}$, find I_{AB} and V_{AB} .

$$I_{AB} = \frac{19.202}{\sqrt{3}} \angle 35 + 30 = 11.086 \angle 65 \text{ A (Line} \rightarrow \text{Phase)}$$

$$V_{AB} = I_{AB} \times Z_{\Delta} = (11.086 \angle 65) \times (18 + j12) = 239.827 \angle 98.69$$

12.5 In a balanced Dell-Y circuit, $V_{ab} = 240 \angle 15$ and $Z_Y = (12 + j15)$ ohm. Calculate the line currents.

$$V_{an} = \frac{V_{ab}}{\sqrt{3}} \angle -30 = \frac{240}{\sqrt{3}} \angle (15 - 30) = 138.56 \angle -15$$

$$I_a = \frac{V_{an}}{Z_Y} = \frac{138.56 \angle -15}{12 + j15} = 7.21 \angle -66.34$$

$$I_b = 7.21 \angle (-66.34 - 120)$$

$$I_c = 7.21 \angle (-66.34 + 120)$$

12.6 For the Y-Y circuit in Practice Prob. 12.2, calculate the complex power at the source and at the load.

At the source,

$$S_s = -3 V_p I_p^* = -3 \times 120 \angle 30 \times 3.75 \angle 8.66 = -1054.17007 - 843.34j \text{ VA}$$

$$S_l = 3 \times |I_p|^2 \times V_l = 3 \times 3.75^2 \times (24 + j19) = 1012.5 + j801.56$$

12.7 Calculate the line current required for a 30-kW three-phase motor having a power factor of 0.85 lagging if it is connected to a balanced source with a line voltage of 440 V.

$$P = S \cos \theta$$

$$\text{or, } S = 30k / 0.85 = 35294.12 \text{ W}$$

$$\text{And, } S = \sqrt{3} \times V_L \times I_L$$

$$\text{or, } I_L = \frac{S}{\sqrt{3} V_L} = \frac{35294.12}{\sqrt{3} \times 440} = 46.31 \text{ A}$$

12.8 Skipped

12.9 The unbalanced Δ -load of Fig. 12.24 is supplied by balanced line-to-line voltages of 240 V in the positive sequence. Find the line currents. Take V_{ab} as reference.

Phase current,

$$I_{AB} = \frac{V_{AB}}{10 - 5j} = \frac{240 \angle 0}{10 - 5j} = 21.46 \angle 26.56$$

$$I_{BC} = \frac{240 \angle -120}{16j} = 15 \angle -120$$

$$I_{CA} = \frac{240 \angle 120}{8 + 6j} = 24 \angle 83.13$$

Line current,

$$I_a = I_{AB} - I_{CA} = 21.46 \angle 26.56 - 24 \angle 83.13$$

$$= 21.66 \angle -41.08 \text{ A}$$

$$I_b = I_{BC} - I_{AB} = 15 \angle -120 - 21.46 \angle 26.56 = 34.88 \angle -140.36 \text{ A}$$

$$I_c = I_{CA} - I_{BC} = 24 \angle 83.13 - 15 \angle -120 = 38.25 \angle 74.27 \text{ A}$$

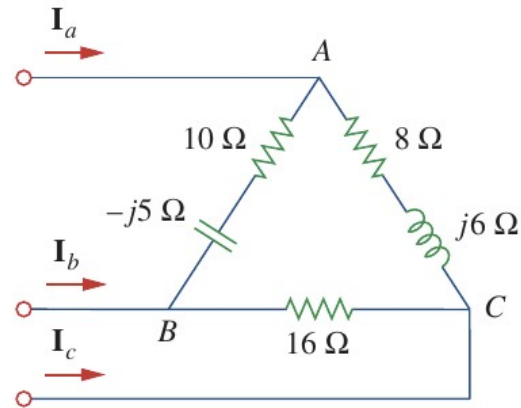


Figure 12.24

Unbalanced Δ -load; for Practice Prob. 12.9.